

Digital Logic Design

Quiz 05


2024/05/07

姓名:

學號:

系級:

1. Implement the following state diagram

 

Hint : present state : $A(t)$; next state : $A(t+1)$; input X, Y ; output Z ;
JK flip-flops inputs : J_A, K_A ;

- (a) Design a **Sequential Circuit** with one **JK flip-flop**. You need to provide the **State Table** (40%), **Equations** (30%) and **Circuit Diagram** (30%).

(a)

State Table

input		PS	NS	output		
x	y	A(t)	A(t+1)	Z	J _A	K _A
0	0	0	1	1	1	X
0	0	1	0	0	X	1
0	1	0	1	0	1	X
0	1	1	1	1	X	0
1	0	0	0	0	0	X
1	0	1	1	0	X	0
1	1	0	0	1	0	X
1	1	1	0	1	X	1

Equation

$$Z = yA(t) + xy + x'y'A(t)'$$

x \ yA(t)		00	01	11	10
0		1		1	
1				1	1

$$J_A = x'$$

x \ yA(t)		00	01	11	10
0		1	X	X	1
1		0	X	X	0

$$K_A = (x \oplus y)'$$

$y \backslash A(t)$	00	01	11	10
0	X	1	0	0
1	X	0	1	X

Circuit Diagram

